

Kap. 26
Likestrømskretser

Målsetning:

Kunne analysere enkle likestrømskretser


Punktvis:

- Resistanser i serie og parallell
- Kirchoffs regler
- RC-kretser


Pensum:

- Y & F kap 26.1 + 2 + 4

Motstander

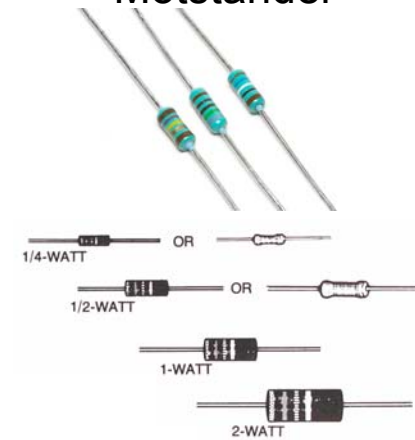


Motstander. Fargekoder.

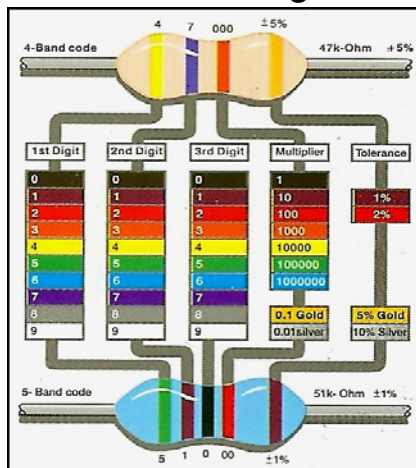


Motstander

Serie: $R = R_1 + R_2 + R_3$

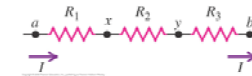


Parallell: $1/R = 1/R_1 + 1/R_2 + 1/R_3$

$G = G_1 + G_2 + G_3$

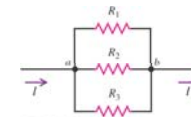


Motsatt for kondensatorer:


Parallell: $C = C_1 + C_2 + C_3$

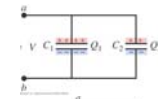

Serie: $1/C = 1/C_1 + 1/C_2 + 1/C_3$

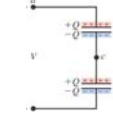

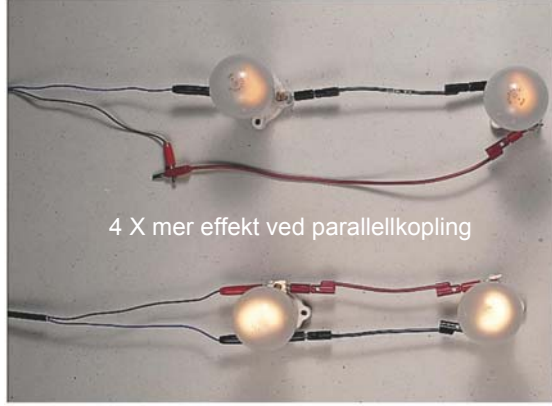
Eks. 1 Effekt i parallell- og seriekopling



4 X mer effekt ved parallellkopling

Copyright © 2008 Pearson Education, Inc., publishing as Pearson Addison-Wesley

Kirchoffs regler

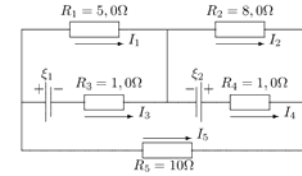


1. Strømløvslov (knutepunktregel): $\sum I_k = 0$




2. Spenningslovslov (maskestrømsregel): $\sum V_k = 0$

OBS fortegn, tenk på spenningsdiagram

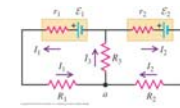

RC-kretser

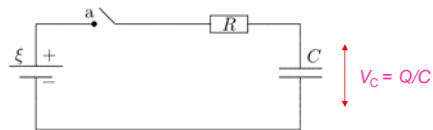

Kondensatorspenning V_C inngår i Kirchoffs maskestrømsregel.

OBS: Q tar tid å endres:

Ladning på kondensator Q kan **ikke** endres brått.

=> Spenning på kondensator $V_C = Q/C$ kan **ikke** endres brått.

Strøm til kondensator $I = dQ/dt$ kan endres brått.

Spenning over motstand $V_R = RI$ kan endres brått.

Strøm $I = V_R / R$ gjennom motstand kan endres brått.

Kap. 26: Likestrømskretser
Oppsummering

Motstander i serie: $R = R_1 + R_2 + R_3$

Motstander i parallell:

Resistans R : $1/R = 1/R_1 + 1/R_2 + 1/R_3$

Konduktans G : $G = G_1 + G_2 + G_3$


Kirchoffs regler:

1. Strømløvslov (knutepunktlov): $\sum I_k = 0$



2. Spenningslovslov (maskestrømslov): $\sum V_k = 0$

OBS fortegn, tenk på spenningsdiagram

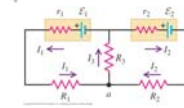

RC-kretser:

Kondensatorspenning V_C inngår i Kirchoffs maskestrømsregel.

V_C og $Q = CV_C$ tar tid å endres:

Spenning på kondensator $V_C = Q/C$ kan **ikke** endres brått.

Strøm til kondensator $I = dQ/dt$ kan endres brått.

Spenning over motstand $V_R = RI$ kan endres brått.