

# Oppgave 1

①

$$a) \omega = 2\pi f = 2\pi \cdot 10^5 \text{ s}^{-1} = \underline{6,28 \cdot 10^5 \text{ s}^{-1}}$$

$$\text{induktiv reaktans } X_L = \omega L = 2\pi \cdot 10^5 \cdot 10^{-3} \Omega = \underline{628 \Omega}$$


$$\text{kapasitiv reaktans } X_C = (\omega C)^{-1} = (2\pi \cdot 10^5 \cdot 10^{-9})^{-1} \Omega = \underline{1592 \Omega}$$

$$\begin{aligned} \text{impedans } Z &= \left( R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right)^{1/2} \\ &= \left( 1000^2 + (628 - 1592)^2 \right)^{1/2} \Omega = \underline{1389 \Omega} \end{aligned}$$

$$I_0 = \frac{V_0}{Z} = \frac{325}{1389} \text{ A} = \underline{0,234 \text{ A}}$$

$$I_{\text{eff}} = \frac{I_0}{\sqrt{2}} = \frac{0,234}{\sqrt{2}} \text{ A} = \underline{0,165 \text{ A}}$$
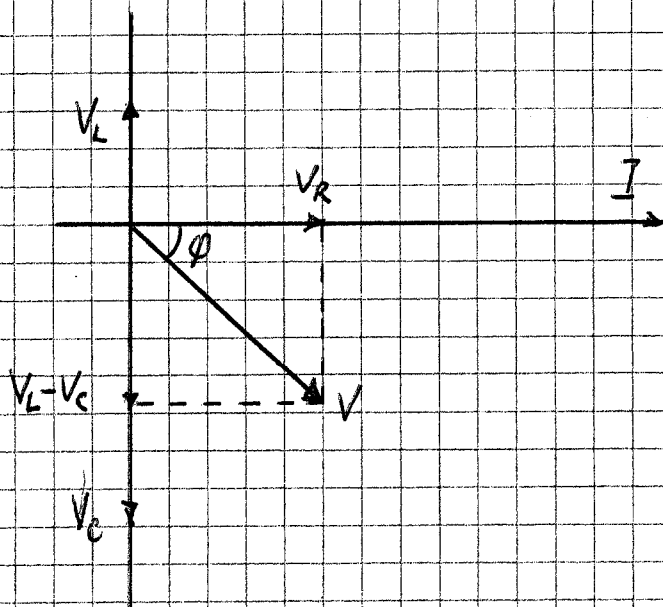
$$\sin \varphi = \frac{\omega L - \frac{1}{\omega C}}{Z} = \frac{628 - 1592}{1389} = \underline{-0,6940} \Rightarrow \varphi = \underline{-43,9^\circ}$$



$$b) I = I_0 \sin \omega t$$

$$P_R = R \cdot I^2 = R I_0^2 \sin^2 \omega t$$

$\langle P_R \rangle$  er  $P_R$  middlet over en periode.

$$\text{Men } \langle \sin^2 \omega t \rangle = \frac{1}{2}$$

$$\Rightarrow \langle P_R \rangle = \frac{1}{2} R I_0^2 = \frac{1}{2} R \frac{V_0^2}{Z^2} = \frac{1}{2} \frac{R}{Z} V_0 \frac{V_0}{Z}$$

$$\frac{R}{Z} = \cos \varphi$$

$$\underline{\langle P_R \rangle = \frac{1}{2} V_0 I_0 \cos \varphi = \langle P \rangle}$$

(3)

c) Når  $\langle P \rangle$  skal være størst mulig, må mest mulig av spenningen ligge over  $R$ , dvs minst mulig må ligge over de andre komponentene, dvs  $Z$  må være minst mulig.

$$Z = \left( R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right)^{1/2} \text{ der } C \text{ er resultat-} \\ \text{kapasitans.}$$

Minst verdi av  $Z$  for  $\omega L = \frac{1}{\omega C}$

$$\Rightarrow C = \frac{1}{\omega L} = \frac{1}{6.28 \cdot 10^{10} \cdot 10^{-3}} \text{ F} = \underline{2.53 \cdot 10^{-9} \text{ F}}$$


$$\Rightarrow C > C_1$$

$$\text{Parallellkobling: } C = C_1 + C_2 \Rightarrow C > C_1$$

$$\text{Seriekobling: } C^{-1} = C_1^{-1} + C_2^{-1} \Rightarrow C < C_1$$

$\Rightarrow$  Parallellkobling
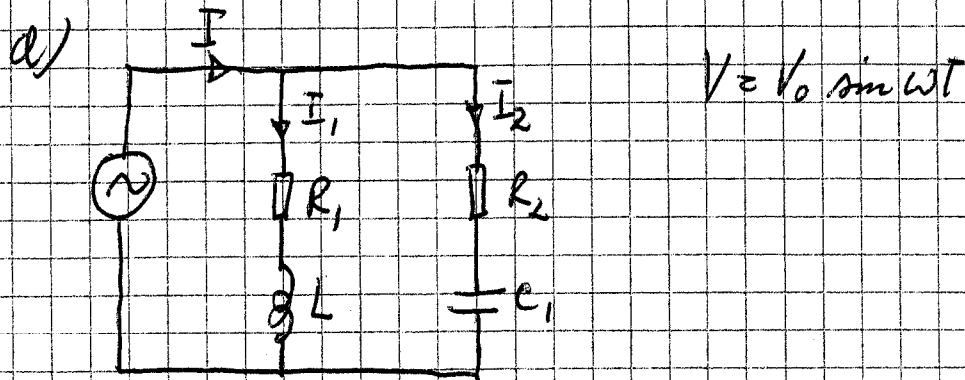
$$C_2 = C - C_1 = (2.53 - 1.00) \text{ nF} = \underline{\underline{1.53 \text{ nF}}}$$



$$Z_1 = (R_1^2 + (\omega L)^2)^{1/2} = (1000^2 + 628^2)^{1/2} \Omega = \underline{1181 \Omega}$$

$$Z_2 = (R_2^2 + (\frac{1}{\omega C_1})^2)^{1/2} = (500^2 + 1592^2)^{1/2} \Omega = \underline{1669 \Omega}$$

Vi giv aktive og reaktive komponenter af strømme indlæser henholdsvis  $p$  og  $q$ .

Vi betragter rms-værdier (effektive værdier).

$$I_1 = \frac{V}{Z_1} = \frac{325}{\sqrt{2} \cdot 1181} \text{ A} = \underline{0,195 \text{ A}}$$

$$I_2 = \frac{V}{Z_2} = \frac{325}{\sqrt{2} \cdot 1669} \text{ A} = \underline{0,138 \text{ A}}$$

$$\sin \varphi_1 = \frac{-\omega L}{Z_1} = \frac{-628}{1181} = -0,5318 \Rightarrow \varphi_1 = \underline{-32,1^\circ}$$

$$\sin \varphi_2 = \frac{1/\omega C_1}{Z_2} = \frac{1592}{1669} = 0,9539 \Rightarrow \varphi_2 = \underline{72,5^\circ}$$

e) Vi gir aktive og reaktive komponenter av strømmene indikerer henholdsvis  $p$  og  $q$ . Vi betrakter rms-verdier (effektivverdier)

$$I_{1p} = I_1 \cos \varphi_1 = 0,195 \cdot \cos(-32,1^\circ) \text{ A} = 0,165 \text{ A}$$

$$I_{1q} = I_1 \sin \varphi_1 = 0,195 \cdot \sin(-32,1^\circ) \text{ A} = -0,104 \text{ A}$$

$$I_{2p} = I_2 \cos \varphi_2 = 0,138 \cdot \cos 72,5^\circ \text{ A} = 0,041 \text{ A}$$

$$I_{2q} = I_2 \sin \varphi_2 = 0,138 \cdot \sin 72,5^\circ \text{ A} = 0,132 \text{ A}$$

$$I_p = I_{1p} + I_{2p} = (0,165 + 0,041) \text{ A} = 0,206 \text{ A}$$

$$I_q = I_{2q} + I_{1q} = (-0,104 + 0,132) \text{ A} = 0,028 \text{ A}$$

$$\bar{I} = (I_p^2 + I_q^2)^{1/2} = (0,206^2 + 0,028^2)^{1/2} \text{ A} = \underline{0,208 \text{ A}}$$

$$\varphi = \arctan(I_q/I_p) = \arctan\left(\frac{0,028}{0,206}\right) \Rightarrow \varphi = \underline{7,7^\circ}$$

(Alternativt: Bruk utvidet Pythagoras)

