

Kap 31: Vekselstrømskretser

31.1 Visere og kompleks notasjon

31.2 (Kompleks) reaktans

31.3 RLC-krets


31.5 Resonans (i RLC-krets)

Kretslover for AC-signal


med eksempel i RLC-seriekrets

Regler:

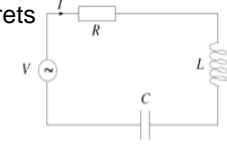- $V(t) = V_0 \cdot e^{i\omega t}$ (1)
- $I(t) = I_0 \cdot e^{i\omega t}$ (2) osv. $V_R(t), V_L(t), V_C(t)$ med lik frekvens ω og komplekse amplituder.




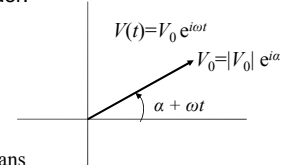- Resistans: $V_R = Z_R I = R \cdot I$ (6)
 $Z_R = R =$ resistans = **resistiv impedans**
- Induktans: $V_L = Z_L I = i\omega L \cdot I$ (7)
 $Z_L = i\omega L =$ **induktiv impedans** $L =$ induktans
- Kapasitans: $V_C = Z_C I = 1/i\omega C \cdot I$ (8)
 $Z_C = 1/i\omega C =$ **kapasitiv impedans** $C =$ kapasitans
- Kirchhoffs lover som vanlig.



OBS:
 $d/dr (e^{i\omega t}) = i\omega e^{i\omega t}$

AC-spenning på RLC-krets

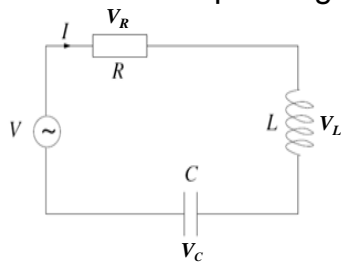

Kirchhoff:
 $V(t) = V_R + V_L + V_C = Z I(t)$ (9)

$$V_R = Z_R I = R \cdot I \quad (6)$$

$$V_L = Z_L I = i\omega L \cdot I \quad (7)$$

$$V_C = Z_C I = 1/i\omega C \cdot I \quad (8)$$

gir seriekretsens komplekse impedans:

$$Z = R + i\omega L + 1/i\omega C$$


$$= R + i(\omega L - 1/\omega C) \quad (10)$$

eller


$$Z = R + Z_L + Z_C$$

(vanlig seriekopling av impedanser)


Detaljer for RL-krets

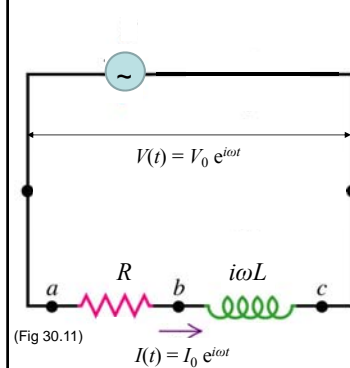

Ohm: $V(t) = Z I(t)$
 impedans $Z = R + i\omega L = |Z| e^{i\phi}$
 (Kompleks) amplitude:
 $V_0(t) = Z I_0(t)$

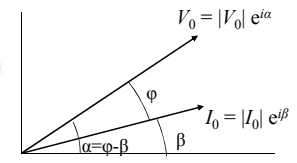

Her:
 velger
 $\beta = 0$


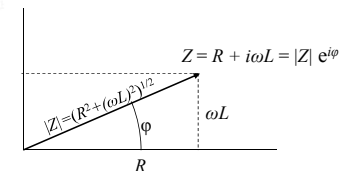


Eks.: RLC-krets

Kirchhoffs spenningslov:

$$V(t) = V_R + V_L + V_C = Z \cdot I(t)$$

gir $Z = R + i\omega L + 1/i\omega C$
 $\Rightarrow |Z| = (R^2 + (\omega L - 1/\omega C)^2)^{1/2}$
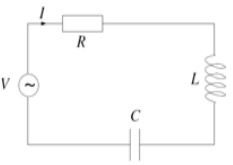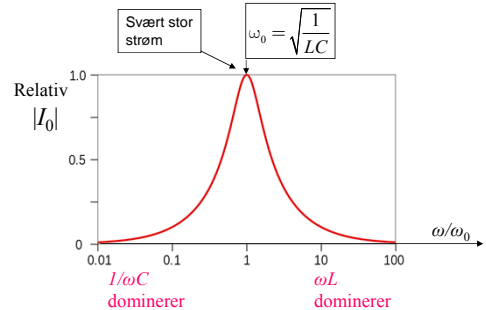
$$I_0 = |V_0|/|Z| \exp(-i\varphi)$$



Relativ $|I_0|$

ω/ω_0

$\omega_0 = \sqrt{\frac{1}{LC}}$

$1/\omega C$ dominerer

ωL dominerer

Svært stor strøm

Eks.: RLC-krets


Kirchhoffs spenningslov:

$$V(t) = V_R + V_L + V_C = Z \cdot I(t)$$


gir $Z = R + i\omega L + 1/i\omega C$
 $\Rightarrow |Z| = (R^2 + (\omega L - 1/\omega C)^2)^{1/2}$

$$I_0 = |V_0|/|Z| \exp(-i\varphi)$$

Med $R = 1/100 \Omega$:

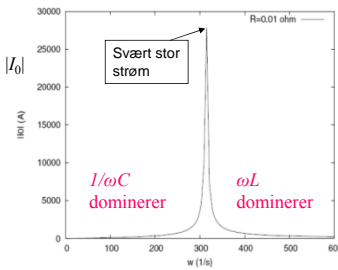

Med $R = 1 \Omega$:

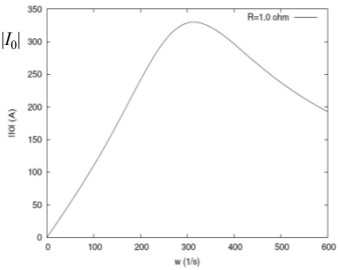

$R=0.01 \text{ ohm}$

$R=1.0 \text{ ohm}$

$1/\omega C$ dominerer



ωL dominerer

Svært stor strøm

Eks: RLC-parallellkrets

Parallellkopling:

$$1/Z = 1/R + 1/i\omega L + i\omega C$$
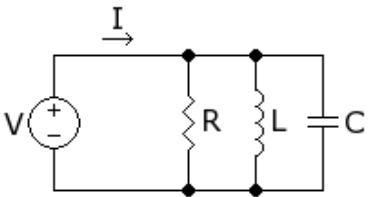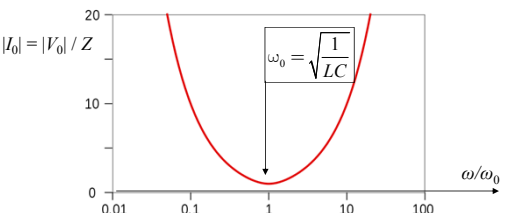
$$Z = \frac{R}{1 + i\left(\omega RC - \frac{R}{\omega L}\right)}$$



$|I_0| = |V_0|/Z$


ω/ω_0

$\omega_0 = \sqrt{\frac{1}{LC}}$

Svært stor strøm

Kompleks impedans med AC-signal

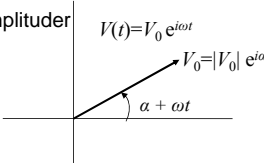- $V(t) = V_0 \cdot e^{i\omega t}$ og $I(t) = I_0 \cdot e^{i\omega t}$ med lik frekvens ω og komplekse amplituder V_0 og I_0 gir en utvidet Ohms lov:
- Resistans: $V_R = Z_R I = R \cdot I$
- Induktans: $V_L = Z_L I = i\omega L \cdot I$
- Kapasitans: $V_C = Z_C I = 1/i\omega C \cdot I$



- Seriekopling: $Z = Z_1 + Z_2$
- Parallellkopling: $1/Z = 1/Z_1 + 1/Z_2$
- Alle kretslover gjelder for AC når Z brukes:
 - Kirchoff 1 (strømlov)
 - Kirchoff 2 (spenningslov)
 - Ohms lov
- OBS: Z gjelder kun AC-signal, ikke andre periodiske signal eller ikke-periodiske signal.