

Oppgave 1

$$a) Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{R^2 + (X_L - X_C)^2}$$

(På kompleks form:  $Z = R + j(\omega L - \frac{1}{\omega C})$ )

$$X_L = 2\pi \cdot 6 \cdot 10^3 \cdot 4 \cdot 10^{-3} \Omega = 150,8 \Omega$$

$$X_C = (2\pi \cdot 6 \cdot 10^3 \cdot 0,4 \cdot 10^{-6})^{-1} \Omega = 66,3 \Omega$$

$$R = 160 \Omega$$

$$Z = \underline{181 \Omega}$$

$$\tan \varphi = \frac{X_L - X_C}{R} = \frac{150,8 - 66,3}{160} = 0,53$$

$$\varphi = \underline{28^\circ}$$

$$I_0 = \frac{V_0}{Z} = \frac{10}{181} \text{ A} = \underline{0,055 \text{ A}}$$

b)

$$V_s = \sqrt{V_R^2 + (V_L - V_C)^2} = I \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$V_{\text{ut}} = \sqrt{V_R^2 + V_L^2} = I \sqrt{R^2 + (\omega L)^2}$$

$$\frac{V_{\text{ut}}}{V_s} = \sqrt{\frac{R^2 + (\omega L)^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \approx \sqrt{\frac{R^2}{\left(\frac{1}{\omega C}\right)^2}} = \underline{\omega RC} \text{ for store } \omega$$

dos  $\frac{V_{\text{ut}}}{V_s}$  tilnærmet proporsjonalt med  $\omega$  for store  $\omega$

For store  $\omega$  er  $\frac{1}{\omega C} \ll \omega L$  og  $\omega L \gg R$ :

$$\Rightarrow \frac{V_{\text{ut}}}{V_s} \approx \sqrt{\frac{(\omega L)^2}{(\omega L)^2}} = \underline{1}$$

(2)

Oppgave 1 forts

$$c) V_s = I \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

$$V_{ut} = V_c = I \cdot \frac{1}{\omega C}$$

$$\frac{V_{ut}}{V_s} = \frac{\frac{1}{\omega C}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

For stor  $\omega$  er  $\frac{1}{\omega C} \ll \omega L$  og  $\omega L \gg R$ :

$$\Rightarrow \frac{V_{ut}}{V_s} \approx \frac{\frac{1}{\omega C}}{\sqrt{(\omega L)^2}} = \frac{1}{\omega^2 LC} \ll \frac{1}{\omega^2}$$

For liten  $\omega$  er  $\frac{1}{\omega C} \gg \omega L$  og  $\frac{1}{\omega C} \gg R$ :

$$\Rightarrow \frac{V_{ut}}{V_s} \approx \frac{\frac{1}{\omega C}}{\sqrt{(\frac{1}{\omega C})^2}} = \underline{1}$$

$$d) r = r_0(1 + \alpha t) \Rightarrow \frac{dr}{dt} = r_0 \cdot \alpha$$

Fluks gjennom ringen:  $\Phi_B = \vec{B} \cdot \vec{A} = B \pi r^2$

$$\text{Indusert emf: } \mathcal{E} = -\frac{d\Phi_B}{dt} = -2\pi B r \cdot \frac{dr}{dt}$$

$$\mathcal{E} = -2\pi B r_0(1 + \alpha t) \cdot r_0 \alpha = -2\pi B r_0^2 \alpha (1 + \alpha t)$$

$$\text{Resistans } R' = R \cdot 2\pi r = R_0(1 + \beta t) \cdot 2\pi r_0(1 + \alpha t)$$

$$\text{Indusert strøm } I = \mathcal{E}/R' = \frac{-2\pi B r_0^2 \alpha (1 + \alpha t)}{R_0(1 + \beta t) 2\pi r_0(1 + \alpha t)}$$

$$I = \frac{-B r_0 \alpha}{R_0(1 + \beta t)}$$

I figuren er strømretningen med klokken.

