

①

$$a) I_3 = 0 \quad I_1 = I_2 = \frac{U}{R_2} = \frac{12}{5} \text{ A} = 2.4 \text{ A}$$

b) Spændingen  $U$  står over  $C_1$

$$\Rightarrow Q = CU = 5 \cdot 10^{-6} \cdot 12 \text{ C} = 60 \mu\text{C}$$

c) Krets med  $R = R_1 + R_2 = (4+5) \Omega = 9 \Omega$   
og  $L = L_1 + L_2 = (50+100) \text{ mH} = 150 \text{ mH}$

$$\frac{Q}{C_1} - RI - L \frac{dI}{dt} = 0$$

$$\frac{Q}{C_1} - R \left( -\frac{dQ}{dt} \right) - L \left( -\frac{d^2Q}{dt^2} \right) = 0$$

$$\frac{d^2Q}{dt^2} + \frac{R}{L} \frac{dQ}{dt} + \frac{Q}{LC_1} = 0$$

$$Q = Q_0 e^{-\alpha t} \cos(\omega t + \varphi)$$

$$\alpha = \frac{R}{2L} \quad \omega = \sqrt{\frac{1}{LC_1} - \frac{R^2}{4L^2}}$$

Oscillerende ladning  $Q$

$$I = -\frac{dQ}{dt} \text{ (ihr pkt e)}$$

$$t=0: Q=Q_0 \Rightarrow \varphi=0$$

Oscillation hvis  $\frac{R^2}{4L^2} < \frac{1}{LC_1} \Rightarrow$  hvis  $R^2 < \frac{4L}{C_1}$

$$R^2 = 9^2 \Omega^2 = 81 \Omega^2$$

$$\frac{4L}{C_1} = \frac{4 \cdot 150 \cdot 10^{-3}}{5 \cdot 10^{-6}} \Omega^2 = 120000 \Omega^2 \Rightarrow R^2 \ll \frac{4L}{C_1}$$

$\Rightarrow$  Krets med oscillerende ladning  $Q$  og oscillerende strøm  $I = -\frac{dQ}{dt}$

$$d) \omega = \sqrt{\frac{1}{LC_1} - \frac{R^2}{4L^2}} = \sqrt{\frac{1}{150 \cdot 10^{-3} \cdot 5 \cdot 10^{-6}} - \frac{9^2}{4 \cdot 150^2 \cdot 10^{-6}}} \text{ s}^{-1}$$

$$= \sqrt{10^6 \cdot 1,333 - 10^6 \cdot 0,00001} = 1,15469 \cdot 10^3 \text{ s}^{-1}$$

$$f = \frac{\omega}{2\pi} = \frac{1,15469 \cdot 10^3}{2\pi} \text{ Hz} = 183,8 \text{ Hz}$$

$$e) Q = Q_0 e^{-\alpha t} \cos \omega t = Q_0 e^{-\frac{R}{2L}t} \cos \omega t \quad (2)$$

$$I = -\frac{dQ}{dt} = -\left[ Q_0 \left(-\frac{R}{2L}\right) e^{-\frac{R}{2L}t} \cos \omega t - Q_0 e^{-\frac{R}{2L}t} \omega \sin \omega t \right]$$

$$= Q_0 e^{-\frac{R}{2L}t} \left( \frac{R}{2L} \cos \omega t + \omega \sin \omega t \right)$$

Men  $\frac{R}{2L} = \frac{9}{2 \cdot 150 \cdot 10^{-3}} \text{ s}^{-1} = 30 \text{ s}^{-1}$  mens  $\omega = 1155 \text{ s}^{-1}$  (påt d.)

$\Rightarrow \frac{R}{2L} \ll \omega$  så det er vi med god tilnærming kan sette  $\omega \approx \frac{1}{\sqrt{LC}}$  (se også alternativ løsning)

$$\Rightarrow I \approx Q_0 e^{-\frac{R}{2L}t} \cdot \frac{1}{\sqrt{LC}} \sin \omega t = I_0 e^{-\frac{R}{2L}t} \sin \omega t$$

$$I_0 = \frac{Q_0}{\sqrt{LC}} = \frac{60 \cdot 10^{-6}}{\sqrt{150 \cdot 10^{-3} \cdot 5 \cdot 10^{-6}}} \text{ A} = \underline{0,0693 \text{ A}}$$

f) Amplituden er halvert når

$$e^{-\alpha t} = e^{-\frac{R}{2L}t} = \frac{1}{2} \Rightarrow -\frac{R}{2L}t = -\ln 2$$

$$t = \frac{2L}{R} \ln 2 = \frac{2 \cdot 150 \cdot 10^{-3}}{9} \ln 2 \text{ s} = 0,0231 \text{ s}$$

$$\text{Perioden } T = \frac{1}{f} = \frac{1}{183,8} \text{ s} = 0,00544 \text{ s}$$

Antall perioder for halvering av amplituden:

$$\frac{t}{T} = \frac{0,0231}{0,00544} \text{ svingninger} = \underline{4,25 \text{ svingninger}}$$

g) Kritisk demping eller overdemping for

$$R^2 \geq \frac{4L}{C}, \text{ dvs for } R \geq \sqrt{\frac{4 \cdot 150 \cdot 10^{-3}}{5 \cdot 10^{-6}}} \Omega = 346 \Omega$$

$$\text{dvs for } R_1 \geq 346 \Omega - R_2 = 346 \Omega - 5 \Omega = \underline{341 \Omega}$$

Alternative for equation c):

$$\frac{Q_0 R}{2L} \cos \omega t + Q_0 \omega \sin \omega t = A \sin(\omega t + \varphi)$$

$$= A \sin \omega t \cos \varphi + A \cos \omega t \sin \varphi$$

$$A \sin \varphi = \frac{Q_0 R}{2L}$$

$$A \cos \varphi = Q_0 \omega$$

$$\tan \varphi = \frac{R}{2L\omega} = \frac{9}{2 \cdot 150 \cdot 10^{-3} \cdot 1155} = 0.02597$$

$$\varphi = \underline{1.49^\circ} = 0.026 \text{ radians}$$

$$A = \frac{Q_0 R}{2L \sin 1.49^\circ} = \frac{60 \cdot 10^{-6} \cdot 9 \text{ A}}{2 \cdot 150 \cdot 10^{-3} \sin 1.49} = 69.2 \cdot 10^{-3} = \underline{0.0692 \text{ A}}$$

Sam viser at approximationen i c) er god.

$$\Rightarrow \underline{I = A \sin(\omega t + \varphi) = 0.0692 \sin(\omega t + 0.026) \text{ A}}$$